

MASTERING FLIP-FLOPS

SR • JK • D • T – Truth Tables,
Characteristic & Excitation Tables

SR

JK

D

T


Flip Flop

A flip-flop is a clock-controlled bistable sequential circuit that can store one bit of information (0 or 1) and changes its output only on the active edge of the clock.

It remembers the last value until the next clock



It is used to build:

 - Registers
- Counters
- Memory
- State machines (FSM)



D Flip Flop

  In D flip flop D stands for Data or delay. It stores the value of D at the clock edge.



Truth table:

D	Q _{n+1}
0	0
1	1

Characteristic table:

D	Q _n	Q _{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Excitation table:

Q _n	Q _{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Characteristic equation: $Q_{n+1} = D$

```

module d_flipflop(
    input d,
    input clk,rst,
    output reg q,qbar
);
always @(posedge clk or posedge rst)
begin
    if(rst) begin
        q<=1'b0;
        qbar<=1'b1;
    end
    else begin
        q<=d;
        qbar<=~d;
    end
end
endmodule

```

```


`timescale 1ns/100ps
module dff_tb;
    reg d;
    reg clk,rst;
    wire q,qbar;

    d_flipflop uut(d,clk,rst,q,qbar);
    always #5 clk = ~clk;
    initial begin
        clk=0; d=0; rst=1;#10;

        rst=0;
        d=0;#10;
        d=1;#10;
        d=0;#10;
        d=1;#10;

    end
endmodule



```

 

T Flip Flop

In T Flip flop T stands for toggle input

  - If $T = 0 \rightarrow$ No change (Hold)
- If $T = 1 \rightarrow$ Toggle (Invert)



Truth table:

T	Q _{n+1}
0	Q _n
1	$\overline{Q_n}$

Characteristic table:

T	Q _n	Q _{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table:

Q _n	Q _{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic equation: $Q_{n+1} = T \oplus Q_n$

```

module t_flipflop(
  input t,
  input clk,rst,
  output reg q,
  output qbar
);

always @(posedge clk or posedge rst) begin
  if(rst)
    q <= 1'b0;
  else
    q <= q^t;
  end
  assign qbar = ~q;
endmodule

```

```

`timescale 1ns/100ps
module tff_tb;
  reg t;
  reg clk,rst;
  wire q,qbar;


  t_flipflop uut(t,clk,rst,q,qbar);
  always #5 clk = ~clk;

  initial begin
    clk=0; t=0; rst=1; #10;
    rst=0;

    t=1; #10;
    t=0; #10;
    t=0; #10;
    t=1; #10;



    end
endmodule

```

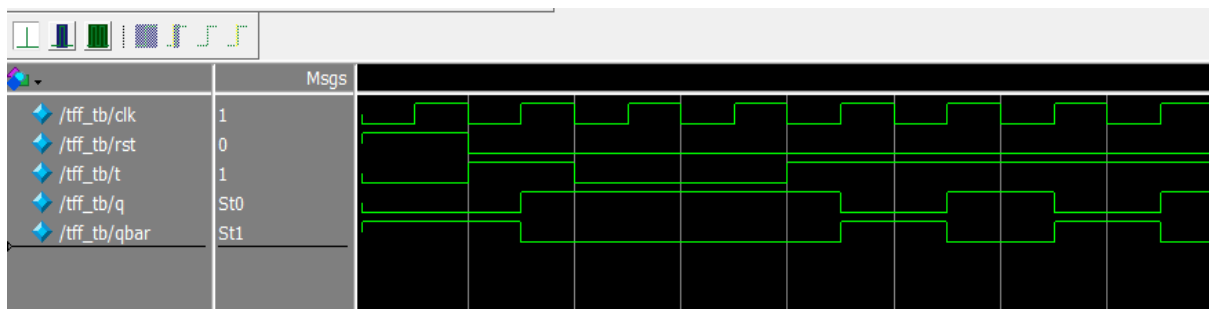

SR Flip Flop

  The SR Flip-Flop (Set–Reset Flip-Flop) is one of the basic memory elements in digital electronics. It is a clock-controlled bistable sequential circuit used to store 1 bit of data (0 or 1).



Truth table:

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	Invalid

S \ R Q(t)	00	01	11	10
0		1		
1	1	1	x	x

$$Q_{n+1} = S + \bar{R}Q_n$$

Characteristic table:

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Excitation table:

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

```

module sr_flipflop(
input s,r,
input clk,rst,
output reg q,
output qbar
);

always @(posedge clk or posedge rst) begin
    if(rst) begin
        q<=1'b0;
    end

    else begin
        case({s,r})
            2'b00: q<=q;
            2'b01: q<=1'b0;
            2'b10: q<=1'b1;
            2'b11: q<=1'bx;
        endcase
    end
end
assign qbar = ~q;
endmodule

```


```

`timescale 1ns/100ps
module srff_tb;
reg s,r;
reg clk,rst;
wire q,qbar;

sr_flipflop uut(s,r,clk,rst,q,qbar);
always #5 clk = ~clk;
initial begin
    clk=0; s=0; r=0; rst=1; #10;
    rst=0;



    s=0; r=0; #10; //memory
    s=0; r=1; #10; //reset
    s=1; r=0; #10; //set
    s=1; r=1; #10; //Invalid in SR
end
endmodule

```

 

JK Flip Flop

  The JK Flip-Flop is an improved version of the SR Flip-Flop that removes the invalid condition ($S=1, R=1$). It is a clock-controlled bistable sequential circuit whose output changes only on the active clock edge.



Truth table:

J	K	Q _{n+1}
0	0	Q _n
0	1	0
1	0	1
1	1	$\sim Q_n$

		KQ _n			
J		00	01	11	10
		0	1	0	0
1	1	1	1	0	1

$$D = J\bar{Q}_n + \bar{K}Q_n$$

Characteristic table:

J	K	Q _n	Q _{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation table:

Q _n	Q _{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

```

module jk_flipflop(
input j,k,
input clk,rst,
output reg q,
output qbar
);

always @(posedge clk or posedge rst) begin
    if(rst) begin
        q<=1'b0;
    end

    else begin
        case({j,k})
            2'b00: q<=q;
            2'b01: q<=1'b0;
            2'b10: q<=1'b1;
            2'b11: q<=~q;
        endcase
    end
end

assign qbar = ~q;
endmodule

```

```

`timescale 1ns/100ps
module jk_tb;
reg j,k;
reg clk,rst;
wire q,qbar;

jk_flipflop uut(j,k,clk,rst,q,qbar);
always #5 clk = ~clk;
initial begin
    clk=0; j=0; k=0; rst=1; #10;
    rst=0;

    j=0; k=0; #10;
    j=0; k=1; #10;
    j=1; k=0; #10;
    j=1; k=1; #10;

end
endmodule

```

